

Switches

Name: _____


Date: _____

Aim: To find out how a switch works.


Equipment I used:




low voltage
lamp

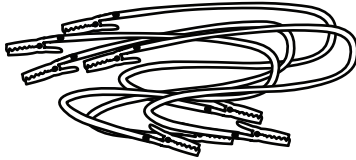


insulated
copper wire

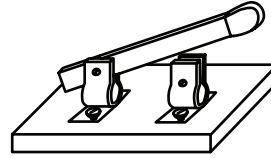

switch

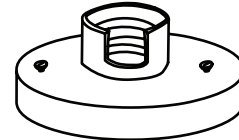

lamp holder


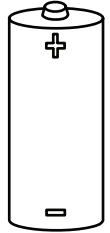


cell

What I did:

What happened:

I discovered that...

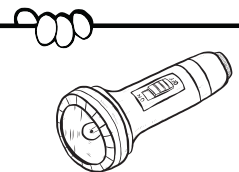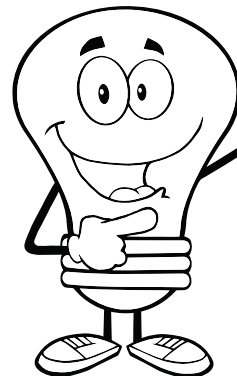

A _____ is used
to control a device
and save battery life.