


Series Circuits

Name: _____

Date: _____

Aim: To find out what happens when two or more lamps are placed in series in a circuit.

Equipment I used:

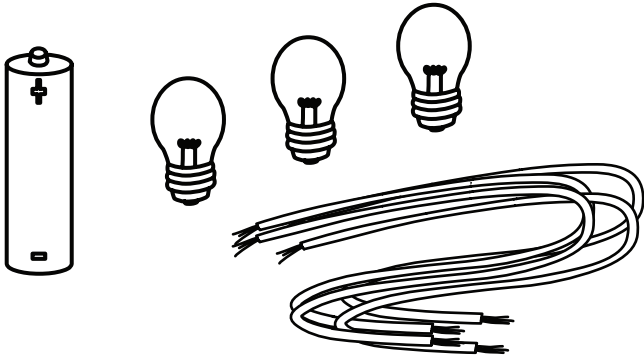

Draw the circuit:

What I did:

What happened:

I discovered that...

